

Ultra low power integer-N ADPLL

Master's thesis project - meeting 7

Cole Nielsen

Department of Electronic Systems, NTNU

28 February 2020 (calendar week 9)

Overview


For this week...

- ① PLL floorplan
- ② Loop filter V2
 - Area/pin location aligned with floor plan.
 - Simplified DSP operation.
 - Changeable filter coefficients.
- ③ Spur estimate.

PLL Floorplan


Loop filter

- Full PLL floorplan necessary to make reasonable placement of pins and to constrain size of loop filter.
- **Total area = 0.0064 mm^2** ($80 \mu\text{m} \times 80 \mu\text{m}$)
 - **Active area = 0.00515 mm^2** (minus DECAP)
- Loop filter architecture simplified to reduce area into $30 \mu\text{m} \times 50 \mu\text{m}$.
- 10b CDAC utilizing minimum $1 \mu\text{m} \times 1 \mu\text{m}$ APMOM caps.
 - Between 1.96-4.72 fF per unit cap (2-4.8 pF total), depending how many metal layers used.
 - Depends on arrangement, however should fit in either $25 \mu\text{m} \times 50 \mu\text{m}$ or perhaps $30 \mu\text{m} \times 50 \mu\text{m}$.
- Include dedicated decap for analog to help with noise?? $25 \mu\text{m} \times 50 \mu\text{m}$ will yield ca. 30 pF.
- Separate power for analog/digital
 - Possibly 0.5 for digital and 0.8 for analog? Higher supply is better for supply rejection with VCO...

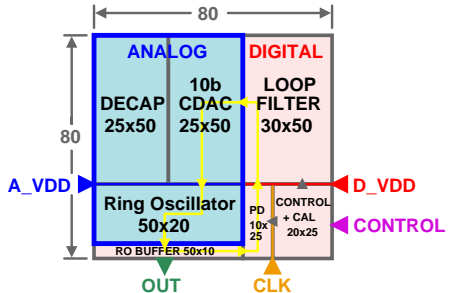


Renewed area comparison.

5nm FinFET state of art

 

- Synthesized PLL in TSMC 5nm FinFET [3] that *has been* fabricated, published in SSCL (2020). Area is 0.0036 mm², or 50 μm x 72 μm.

MDLL State of art

 

- Figure from 2019 JSSC paper [2] on a MDLL. Area is 0.0056 mm^2 in 28nm technology.
- FOM_r here is with normalization to a 200 MHz reference oscillator.
- This work uses higher power (1.45 mW), and higher reference (200 MHz), which perhaps explains better FOM.


Verdict: Competitive in area with state of art (not revolutionary though).

New loop filter.


PI-only with changeable filter coefficients.

- Original architecture with 2 feedforward/2 feedback filter coefficients becomes large (ca. $60\ \mu\text{m} \times 60\ \mu\text{m}$).
 - Implemented fixed pole at zero, and one each of tunable pole/zeros.
 - With N bit word size, requires $4 \times N \times N$ array multiplier.
- **Solution:** reduce to only two feedforward programmable filter coefficients. **This is a classical PI-controller.**
 - Stability is straightforward, PLL dynamics simpler to model.
 - Uncompensated zero results in inherent peaking of phase noise spectrum.
- **Also implemented:** On-the-fly changeable filter coefficients to allow for gear switching of the PLL.

Old Loop Filter (PI + tunable pole)

 

New Loop Filter (PI-only)

 


New loop filter.

PI-only with changeable filter coefficients.

- Current filter optimization yields the following minimum resolution requirements:

Mode	Sign	Integer	Fractional	Sum
Counter	1	4	5	10
BBPD	1	4	11	16

 
- Selection of the input word size x_{in} has been made to equal the counter resolution (8 bit). Accounting for a sign bit this equates to 7 integer bits.
- **Also implemented:** On-the-fly changeable decimal location to allow for gear switching of the PLL.



New loop filter.


New split architecture.

 - Now use split datapath for counter and BBPD modes.
- Reducing to only two feed forward coefficients allows for removal multipliers for BBPD use.
 - Now implemented with muxes.
 - Lower power/complexity, can use larger word for filter coefficients (24 bit) with little penalty, ie. adder complexity is $\mathcal{O}(n \log n)$, vs $\mathcal{O}(n^2)$ for multipliers.



BBPD-PLL resolution jitter



Resolution/phase quantization effects

 

- Output of BBPD is quantized ± 1 . With PI loop filter architecture, there are only 4 possible values that the output w can increment by: $\lfloor b_0 + b_1 \rfloor$, $\lfloor b_0 - b_1 \rfloor$, $\lfloor -b_0 + b_1 \rfloor$, $\lfloor -b_0 - b_1 \rfloor$.
- In steady state, with the BBPD outputting a worst case sequence of $+1/-1/+1/-1\dots$, the output will toggle between $\lfloor b_0 - b_1 \rfloor$ and $\lfloor -b_0 + b_1 \rfloor$.
 - Current optimization yields $b_0 = 8.899856$, $b_1 = -8.301153$
 - Thus output w will increment by $+17, -18, +17, -18 \dots$
 - Essentially output will make large-ish jumps in frequency every reference cycle

BBPD-PLL resolution jitter

Worst case estimate (for spurs)

  

- Worst case input sequence results in square wave frequency modulation, which in the phase domain creates a cyclo-stationary triangle wave with period $f_{ref}/2$. This creates **SPURS** at $f_{ref}/2$.
- In general, $f_{ref} \gg K_{DCO}|b_0 - b_1|$ (frequency deviation), so spurs are not generated at the deviation frequencies.
- With 1 LSB deviation per ref. cycle, a -62 dBc spur (SSB) is expected $f_{ref}/2$.
 - Under my current b_0, b_1 , this spur will be -37 dBc.

BBPD-PLL resolution jitter

Total phase noise estimate from resolution jitter.

— Cyclostationary (+1, -1, +1, -1, ...):

- Under my system parameters, the total phase noise power from resolution effects is -34 dBc, essentially all of which is in the first spur at $f_{ref}/2$.

$$\Delta\Phi = \frac{2\pi|b_0 - b_1|K_{DCO}}{f_{ref}} \quad (1)$$

$$\sigma_{\Phi rj} = \frac{\pi|b_0 - b_1|K_{DCO}}{\sqrt{3}f_{ref}} \quad (2)$$

- **General note:** the phase noise from this source must \ll than target SNR for PLL application. Can use these relations to find limits for maximum K_{DCO} before resolution jitter is dominant.



BBPD-PLL resolution jitter

Total phase noise estimate from resolution jitter.

— Average case:

- All transitions equally likely out of BBPD.
- Under my system parameters, the total phase noise power from resolution effects is -29.4 dBc (simulated).
- Phase noise is bimodal. The total RMS phase noise power is approximately equal to the absolute value of the distribution means.

$$\mu = \pm \frac{\pi |b_0 - b_1| K_{DCO}}{f_{ref}}, \quad \sigma_{\Phi_{rj}} \approx |\mu| \quad (3)$$

  

BBPD Gain.

Additional nonlinearity to an already nonlinear thing...

- Found an interesting dissertation on BBPD PLLs [3], which shows that the linearized BBPD gain model I have been using ($K_{BBPD} = 2 / \sqrt{2\pi} \sigma_{\Phi n}$) is not totally correct.
 - Due to BBPF-PLL resolution jitter, varies depending if resolution jitter or if random noise is the dominant component.
- Need to account for this in my filter optimization code...
- An approximation, with random/uncorrelated noise with $\sigma_{\Phi UC}$, and resolution jitter $\sigma_{\Phi rj}$ (based on variable substitution of [3]'s theory):

$$K_{BBPD} = \frac{1}{\sqrt{2\pi} \sigma_{\Phi UC}} \left[1 + e^{-\frac{1}{2} \left(\frac{\sigma_{\Phi rj}}{\sigma_{\Phi UC}} \right)^2} \right] \quad (4)$$

$$\sigma_{\Phi rj} \approx \frac{\pi |b_0 - b_1| K_{DCO}}{f_{ref}} \quad (5)$$

- Currently, I should be well into the random noise dominated regime.

 



Figure 4.5: Plot of K_{bpd} versus σ_{tjr} (gaussian jitter, $N\beta K_T$ normalized to 1): K_{bpd} computed with a 101 states Markov Chain (thick solid), K_{bpd} approximated with a 3 states Markov Chain (thick dashed), asymptote $K_{bpd} = 1/(\sqrt{2\pi}\sigma_{tjr})$ (thin solid), asymptote $K_{bpd} = 2/(\sqrt{2\pi}\sigma_{tjr})$ (thin dashed).

Filter optimization

Need to add

- ① Modeling of BBPD jitter (extracted from circuit simulation).
- ② Account for noise from limit cycle/phase resolution effects.
 - Adjust K_{BBPD} accordingly
- ③ Aliasing/folding of high frequency phase noise into bandwidth of f_{ref} due to sampled nature
 - Impossible to avoid...

 
Can maybe get better correlation between filter optimization results and discrete time simulation.



Synthesis/place and route


Loop filter layout.

 — First iteration at loop filter layout... still need to extract the circuit/LVS etc...



Architecture

Block Diagram

 

Power Targets (revised)

(Divider not necessary)

DCO	Phase detector	Digital (LF)	Other	SUM
50 μ W	10 μ W	10 μ W	$0 \leq 5 \mu$ W	$\leq 70 + 100 \mu$ W

Specification

System Performance Targets

Parameter	Value	Unit	Notes
Frequency	2.4-2.4835	GHz	2.4G ISM Band
Ref. frequency	16	MHz	Yields 6 channels
Power	≤ 70 75 μW	μW	Minimize!
FSK BER	$\leq 1\text{e-}2$		GFSK* with $f_{dev} = \pm 250$ KHz
CNR	> 20	dBc	Yields -235 dB FOM _{jitter} ideally
Initial Lock Time	≤ 10	μs	Upon cold start
Re-lock Time	≤ 5	μs	Coming out of standby, $f_{error} < 1$ MHz
Lock Δf tolerance	100	kHz	
FOM _{jitter}	≤ -230	dB	For state of art in size/power
Area	< 0.01	mm^2	

* Using BT=0.3, 1 MSymbols/s, 4 demodulated symbols averaged per bit to yield 250 kbps.

Specification

Component-level specs

Parameter	Value	Unit
Counter range	256 steps	coverage of 150-155
Divider ratio	150-155	(For non-counter based)
TDC-resolution	≥ 155	steps/reference cycle
DCO gain K_{DCO}	10^4	Hz/LSB
DCO tuning range	10	MHz
DCO DAC resolution	10	bit
DCO Phase noise	< -80	dBc/Hz @ $\Delta f = 10^6$ Hz, $f_c = 2.448$ GHz
DCO Power	≤ 50	μW
Digital filter word resolution	≤ 16	bits (power grows as $\mathcal{O}(n^2)$)
BB-PD jitter	≤ 12	ps _{rms}

Time plan (pt. 1)

Week #	Dates	Tasks	Outcomes
4	20.1 - 26.1	Finalize high level modeling	Component level specification
5	27.1 - 2.2	Establish test bench in Virtuoso	With ideal PLL implementation
6	3.2 - 9.2	Schem. design: phase detector	TDC - flash and counter based
7	10.2 - 16.2	Schem. design: phase detector	Bang-bang phase detector
8	17.2 - 23.2	RTL, synthesis, place&route	Digital loop filter
9	24.2 - 1.3	RTL, synthesis, place&route	Digital loop filter
10	2.3 - 8.3	Schem. design: oscillator	Ring DCO
11	9.3 - 15.3	Layout: oscillator	
12	16.3 - 22.3	CDAC	Schem+layout
13	23.3 - 29.3	Calibration	RTL/schem. for calibration
14	30.3 - 5.4	Flex week - schem. design	Finalize schematic level design
15	6.4 - 12.4	Easter	-
16	13.4 - 19.4	Layout	Phase detector
17	20.4 - 26.4	Layout	Oscillator

Legend: Done Current Revised

Time plan (pt. 2)

Week #	Dates	Tasks	Outcomes
18	27.4 - 3.5	Layout	Divider/calibration
19	4.5 - 10.5	Layout	Finalization/system integration
20	11.5 - 17.5	Flex week (layout) OR yield improvement	Depending on progress
21	18.5 - 24.5	Report writing	
22	25.5 - 31.5	Report writing	
23	1.6 - 7.6	Report writing	Deadline 8.6

Legend: Done Current Revised

References

- [1] Liu, B., Li, Z., Fu, X., Shirane, A., Kurosu, H., Nakane, Y., Masaki, S., Okada, K., Zhang, Y., Qiu, J., Huang, H., Sun, Z., Xu, D., Zhang, H., Wang, Y. and Pang, J. (2020). A Fully-Synthesizable Fractional-N Injection-Locked PLL for Digital Clocking with Triangle/Sawtooth Spread-Spectrum Modulation Capability in 5 nm CMOS. IEEE Solid-State Circuits Letters, pp.1-1.
- [2] Yang, S., Yin, J., Mak, P. and Martins, R. (2019). A 0.0056-mm² -249-dB-FoM All-Digital MDLL Using a Block-Sharing Offset-Free Frequency-Tracking Loop and Dual Multiplexed-Ring VCOs. IEEE Journal of Solid-State Circuits, 54(1), pp.88-98.
- [3] N. Da Dalt, "Linearized analysis of a digital bang-bang PLL and its validity limits applied to jitter transfer and jitter generation", IEEE Trans. Circuits Syst. I, vol. 55, pp. 3663-3675, Dec. 2008.