

Ultra low power integer-N ADPLL

Master's thesis project - meeting 4

Cole Nielsen

Department of Electronic Systems, NTNU

7 February 2020 (calendar week 6)

Overview


For this week...

- ① Theory for optimal PLL using BB-PD.
- ② Linear phase detector
 - Delay line methods waste of time, need calibration, complexity increases with resolution
 - Counter TDC is viable.

Noisy BB-PD Model.


Introduction of timing jitter to model.

 - Uncorrelated / stochastic processes in a BB-PD result in the $\mathbb{E}[Z]$ with respect to input timing difference Δt_{xy} to deviate from an ideal step response.
- $d\mathbb{E}[Z]/d\Delta t_{xy}$ results in a timing jitter probability distribution $P(T=\Delta t_{xy})$. The variance of this distribution on random jitter variable T , $\text{Var}[T] = \sigma_{t,j}^2$, is the jitter power.



Noisy BB-PD Model.

Linearized noisy BB-PD model.

 

- BB-PD is non-linear, however with a stationary input ϕ_e with power $\sigma_{\phi_e}^2$, its gain can be linearized [1] as:


$$K = \sqrt{\frac{2}{\pi}} \cdot \frac{1}{\sigma_{\phi_e}} \quad (1)$$

- The output has power $\sigma_{\phi_Z}^2 = 1 = K^2 \sigma_{\phi_e}^2 + \sigma_{\phi_{q,bbpd}}^2$
- $\phi_{q,bbpd}$ is a error noise power inherent to the BB-PD.

$$\sigma_{\phi_{q,bbpd}}^2 = 1 - \frac{2}{\pi} \quad (2)$$

Noisy BB-PD Model.

 Linearized noisy BB-PD model (continued).



- Referring $\phi_{q,bbpd}$ to be before gain K, results in a total phase noise power for the BB-PD (assuming all noise sources uncorrelated):

$$\sigma_{\phi_n, BBPD}^2 = \left(\frac{\pi}{2} - 1 \right) \sigma_{\phi_e}^2 + \frac{\pi}{2} \sigma_{\phi_j}^2 \quad (3)$$

- If the BB-PD is connected directly to oscillator output, $\sigma_{\phi_e}^2 = \sigma_{\phi_n}^2$, i.e. the PLL output phase noise. The spectral density of the BB-PD phase noise is then:

$$S_{\phi_n, BBPD} = \frac{\sigma_{\phi_n, BBPD}^2}{f_{ref}} = \frac{\left(\frac{\pi}{2} - 1 \right) \sigma_{\phi_n}^2 + \frac{\pi}{2} \sigma_{\phi_j}^2}{f_{ref}} \quad (4)$$

BB-PD PLL Optimization.



Approximate model for phase noise and optimal bandwidth.

- It is observed that PLL phase noise spectrum is approximately Lorentzian (except for peaking and flicker noise components). Given BB-PD noise PSD of $S_{\phi n, BBPD}$, and an oscillator with noise PSD $S_{\phi n, osc}(\Delta f)$, the optimal bandwidth for minimum noise power is:

$$BW_{opt} = \sqrt{\frac{S_{\phi n, osc}(\Delta f)}{S_{\phi n, BBPD}}} \Delta f \quad (5)$$

- The total PLL output phase noise with optimal bandwidth is then:
  
$$\sigma_{\phi n, opt}^2 = \pi \sqrt{\phi_{n, osc}(\Delta f) S_{\phi n, BBPD}} \Delta f \quad (6)$$



BB-PD PLL Optimization.

BB-PD Jitter constraint with fixed BW and f_{ref} relationship.

- Using the findings for BB-PD noise PSD, assumption of Lorentzian spectrum, and constraint that $BW = \alpha f_{ref}$ (recommended $\alpha < 0.1$ [2], rule of thumb since ancient PLL days). Given oscillator center frequency f_c , BB-PD jitter is constrained:

$$\sigma_{tj} \leq \frac{\sigma_{\Phi n}}{2\pi f_c} \sqrt{\frac{2}{\pi} \left(\frac{1}{\pi \alpha} - \frac{\pi}{2} + 1 \right)} = \frac{\sigma_{\Phi n}}{2\pi f_c} \beta(\alpha) \quad (7)$$

- $\beta(\alpha = 0.1) = 1.28$, $\beta(\alpha = 0.05) = 1.92$.
- Using my PLL specifications ($f_c = 2.448$ GHz, $CNR = -\sigma_{\Phi n} = 17$ dB, $\alpha = 0.1$), $\sigma_{tj} \leq 11.8$ ps

BB-PD optimal Jitter.

- With an unconstrained relationship for BW and f_{ref} , and the optimal bandwidth finding, it is determined that the optimal value of σ_{tj} for minimum phase noise is:

$$\sigma_{tj,opt} = \frac{\sigma_{\Phi n}}{2\pi f_c} \sqrt{\frac{2}{\pi} \left[\frac{\sigma_{\Phi n}^4 f_{ref}}{\pi^2 S_{\phi n,osc}(\Delta f) \Delta f^2} - \left(\frac{\pi}{2} - 1 \right) \sigma_{\Phi n}^2 \right]} \quad (8)$$

BB-PD PLL Optimization.

Optimal parameter selection.

- Setting the two jitter equations of the last slide equal, it is found that optimal phase noise power is:

$$\sigma_{\Phi_n, opt}^2 = \frac{\pi S_{\phi_n, osc}(\Delta f) \Delta f^2}{\alpha f_{ref}} \quad (9)$$

- The optimal reference frequency ($\sigma_{\Phi_n} = 2\pi f_c \sigma_{t_n} = \text{CNR}$):

$$f_{ref} = \frac{\pi S_{\phi_n, osc}(\Delta f) \Delta f^2}{\alpha \sigma_{\Phi_n}^2} \quad (10)$$

- The optimal oscillator phase noise at offset Δf :

$$S_{\phi_n, osc}(\Delta f) = \frac{\alpha f_{ref} \sigma_{\Phi_n}^2}{\pi \Delta f^2} \quad (11)$$

- For CNR = 17 dB, $S_{\phi_n, osc}(\Delta f = 1\text{MHz}) = -80\text{ dBc/Hz}$, $\alpha = 0.1$, the optimal $f_{ref} = 15.7\text{ MHz}$.
- For CNR = 20 dB, $S_{\phi_n, osc}(\Delta f = 1\text{MHz}) = -80\text{ dBc/Hz}$, $\alpha = 0.1$, the optimal $f_{ref} = 31.4\text{ MHz}$.


TDC implementation

Architectures

- Two choices for coarse linear phase detector, delay line TDC or synchronous counter.
- **Coarse delay line TDC**
 - (-) Complexity grows as $\mathcal{O}(n)$.
 - (-) Requires calibration of delay cells (possibly slow).
 - (-) Linearity issues, with poor calibration, gain accuracy is a problem.
 - (-) Needs divider.
- **Synchronous counter**
 - (+) Complexity grows as $\mathcal{O}(\log(n))$.
 - (+) No calibration, no linearity issues.
 - (+) Divider not needed (reduces noise, power?).
 - (-) High power, must run as oscillator frequency.
 - (-) Resolution limited be to equal to divider modulus.
- Counter approach has *significant* advantages for PLL start up. Will switch of counter after initial lock to save power.

Digital TDC

Coarse Delay line (BAD)

 



- Standard N-stage inverter-based delay line.
- Complexity is problematic, $\mathcal{O}(n)$.
- Use mux to allow for delay line to operate as ring oscillator for calibration.
- Over N reference cycles in ring oscillator mode, a delta in the output word of ΔTDC corresponds to the following gain accuracy of the TDC (use to calibrate):

$$\frac{\Delta t_{line}}{T_{ref}} = \frac{\Delta TDC(N_{CYCLES})}{M \cdot N_{CYCLES}} \quad (12)$$

Flip flop for counter schematic

True single phase circuits


- I have implemented the divider using enhanced true single phase clock circuit (E-TSPC) DFFs. These are preferred in PLLs as they provide good energy-delay characteristics, but are not used in logic as the signal quality isn't perfect/limited retention time.
- These are implemented in minimum size for DFM ruleset (100nm/20nm) in SLVT.
- e-TSPC DFF is typically 6 transistors, I have added 1 transistor to implement asynchronous reset and one inverter to get an inverted output.

  

Synchronous counter power


Swept Vdd

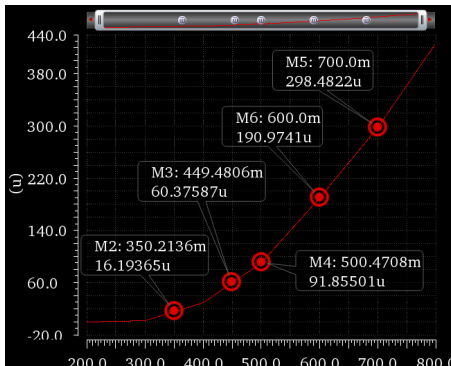- Power grows rapidly with Vdd. For $< 50 \mu\text{W}$, should keep Vdd $< 430 \text{ mV}$.
- Cmin = 10 aF .



Synchronous counter output



400 mV Vdd

 

Importance of counter power.

Monte-Carlo simulation of lock time.



- Monte-Carlo simulation with 1000 samples, 20% RMS deviation in K_{DCO} , and 60 MHz (2.5% of nominal) RMS deviation in initial frequency error. Gear switch used for fast locking. **Mean lock time of 6 μs .**
- **High counter power consumption is not problematic.** If PLL on time = 256 μs , counter power is 5x the BB-PD, and the counter is disabled after gear 1 lock, averaged power increases only 9% versus BB-PD alone (i.e. 10 μW \rightarrow 11 μW).

  

Wrapper for transistors?


Attempt...

  - Trond mentioned before that for a master's project, we should create a sort of wrapper for the transistors to improve portability.
- Should this be fixed unit size device, or can I implement it with pass-through of parameters to the symbol from the technology library (as I have currently done)?
- Also, I will use the 5/6 terminal devices in my schematics (with parasitic diodes for the wells).



Architecture

Block Diagram

 

Power Targets (revised)

(Divider not necessary)

DCO	Phase detector	Divider	Digital (LF)	Other	SUM
50 μ W	10 μ W	N/A 10 μW	10 μ W	≤ 5 10 μ W	≤ 75 100 μ W

Specification

System Performance Targets

Parameter	Value	Unit	Notes
Frequency	2.4-2.4835	GHz	2.4G ISM Band
Ref. frequency	16	MHz	Yields 6 channels
Power	≤ 75 100 μW	μW	Minimize!
FSK BER	$\leq 1\text{e-}2$		GFSK* with $f_{dev} = \pm 250$ KHz
CNR	> 20	dBc	Yields -235 -233 dB FOM _{jitter} ideally
Initial Lock Time	≤ 10	μs	Upon cold start
Re-lock Time	≤ 5	μs	Coming out of standby, $f_{error} < 1$ MHz
Lock Δf tolerance	100	kHz	
FOM _{jitter}	≤ -230	dB	For state of art in size/power
Area	< 0.01	mm^2	

* Using BT=0.3, 1 MSymbols/s, 4 demodulated symbols averaged per bit to yield 250 kbps.

Specification

Component-level specs

Parameter	Value	Unit
Counter range	256 steps	coverage of 150-155
Divider ratio	150-155	(For non-counter based)
TDC-resolution	≥ 155	steps/reference cycle
DCO gain K_{DCO}	10^4	Hz/LSB
DCO tuning range	10	MHz
DCO DAC resolution	10	bit
DCO Phase noise	< -80	dBc/Hz @ $\Delta f = 10^6$ Hz, $f_c = 2.448$ GHz
DCO Power	≤ 50	μ W
Digital filter word resolution	≤ 16	bits (power grows as $\mathcal{O}(n^2)$)
BB-PD jitter	≤ 12	ps _{rms}

Time plan (pt. 1)

Week #	Dates	Tasks	Outcomes
4	20.1 - 26.1	Finalize high level modeling	Component level specification
5	27.1 - 2.2	Establish test bench in Virtuoso	With ideal PLL implementation
6	3.2 - 9.2	Schem. design: phase detector	TDC - flash and counter based
7	10.2 - 16.2	Schem. design: phase detector	Bang-bang phase detector
8	17.2 - 23.2	RTL, synthesis, place&route	Digital loop filter
9	24.2 - 1.3	RTL, synthesis, place&route	Digital loop filter
10	2.3 - 8.3	Schem. design: oscillator	Ring DCO
11	9.3 - 15.3	Schem. design: oscillator	LC DCO
12	16.3 - 22.3	Schem. design: divider	TSPC + pulse swallow or sync counter?
13	23.3 - 29.3	Schem. design: Calibration	RTL/schem. for calibration
14	30.3 - 5.4	Flex week - schem. design	Finalize schematic level design
15	6.4 - 12.4	Easter	-
16	13.4 - 19.4	Layout	Phase detector
17	20.4 - 26.4	Layout	Oscillator

Legend: Done Current Revised

Time plan (pt. 2)

Week #	Dates	Tasks	Outcomes
18	27.4 - 3.5	Layout	Divider/calibration
19	4.5 - 10.5	Layout	Finalization/system integration
20	11.5 - 17.5	Flex week (layout) OR yield improvement	Depending on progress
21	18.5 - 24.5	Report writing	
22	25.5 - 31.5	Report writing	
23	1.6 - 7.6	Report writing	Deadline 8.6

Legend: Done Current Revised

References

- [1] H. Xu and A. A. Abidi, "Design Methodology for Phase-Locked Loops Using Binary (Bang-Bang) Phase Detectors," IEEE Transactions on Circuits and Systems I: Regular Papers, vol. 64, no. 7, pp. 1637–1650, Jul. 2017.
- [2] F. Gardner, "Charge-Pump Phase-Lock Loops," IEEE Transactions on Communications, vol. 28, no. 11, pp. 1849–1858, Nov. 1980, doi: 10.1109/tcom.1980.1094619.